


Neutron Monitor Workshop 2(A): Principles of Digital Logic



Mahidol University

June 25, 2009

 Paul Evenson
University of Delaware
Bartol Research Institute



Workshop Series Idea



- Introduce students to technical aspects of neutron monitor operation
- Rotating workshop series that will repeat every two years at a two per year rate
- Independent enough so students can join at any point
- Accommodate wide skill range with an emphasis on “hands on” experience and individual discussion

Workshop Series Plan



1. Detector operation
 - A. Detector Physics and Analog Electronics
 - B. Art and Science of Soldering
2. Digital Circuits
 - A. Principles of Digital Logic
 - B. Neutron Monitor Digital Electronics
3. Microcontrollers (including data transfer methods within the electronics system)
4. Real time data acquisition
 - A. Principles of Telemetry and Data Acquisition
 - B. Data Conversion and Manipulation with Visual Basic

Plan For Today




- Lecture with Demonstrations
 - Questions and answers
- Describe Design Problems
 - Questions and answers
- Individual work on design problems
 - Only one prototype system here
 - Limited number of parts
 - Testing your design will be left for later

Digital Circuits




- Ultimately composed of the same type of electronic components as analog electronics
- Digital signals are expressed as analog levels
- Typically there are only two logic levels
 - Called “0” and “1”; “Low” and “High”
 - Low is usually near ground
 - High is usually near supply voltage (often +5 volts)
 - (Bad practice to use supply itself for “High”)
- One could define a range of discrete levels but typically this is not done

Simplest Logic Elements

 

 - Buffer: Really doesn't do anything except isolate the input signal and condition the output




- Inverter: The circle on an input or output indicates inversion


AND and NAND



A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

 

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

 


- Note that you can make *any* logic function out of NAND gates




OR and NOR



A	B	Out
0	0	0
0	1	1
1	0	1
1	1	1

 

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

   


- You can also make *any* logic function out of NOR gates
- OR, NOR, AND, NAND all have natural multi-input extensions

XOR (Exclusive OR)




A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

 

- This is the “even parity” operation
- Multi input operation is not well defined
 - One and only one?
 - Odd number?
 - All but one?



Simple Implementations

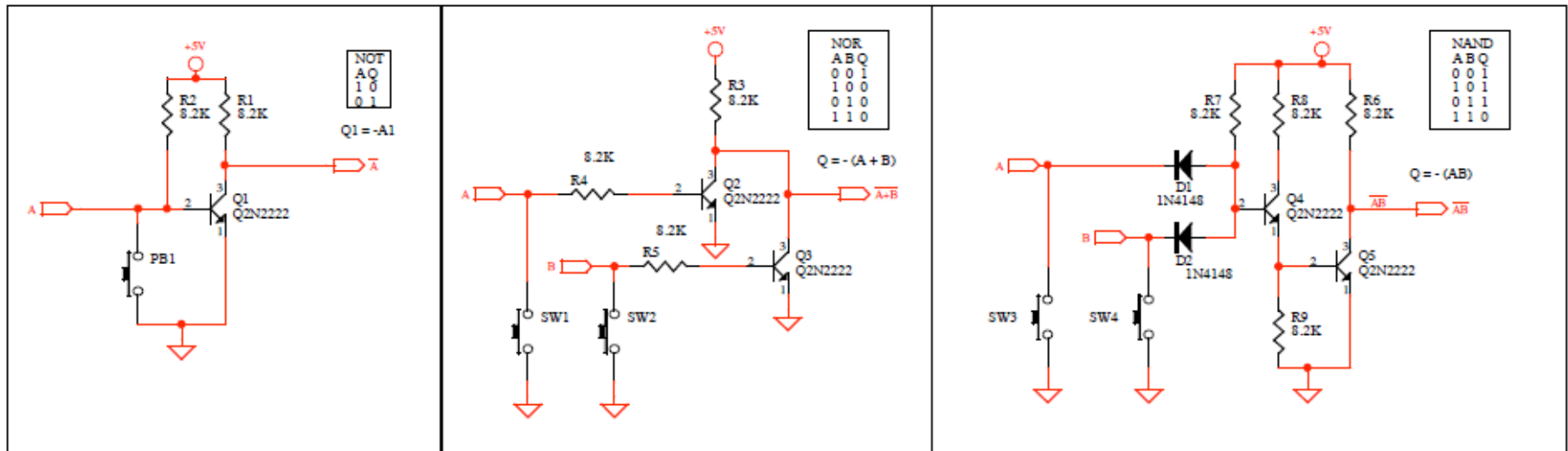

- Note that these work, but they are poorly buffered on inputs and outputs, and cannot be combined easily into more complex circuits

Device Properties

74HC00; 74HCT00 Quad 2-input NAND gate



PINNING

PIN	SYMBOL	DESCRIPTION
1	1A	data input
2	1B	data input
3	1Y	data output
4	2A	data input
5	2B	data input
6	2Y	data output
7	GND	ground (0 V)
8	3Y	data output
9	3A	data input
10	3B	data input
11	4Y	data output
12	4A	data input
13	4B	data input
14	V _{cc}	supply voltage

 
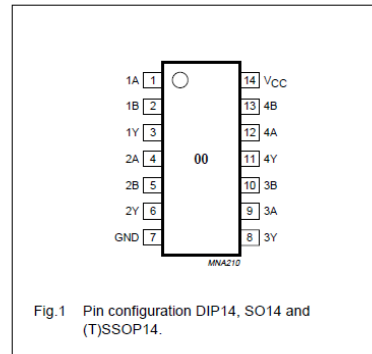


Fig.3 Logic diagram (one gate).

 


Fig.4 Function diagram.

Key DC Design Parameters



Philips Semiconductors

Product specification

Quad 2-input NAND gate

74HC00; 74HCT00

SYMBOL	PARAMETER	TEST CONDITIONS		MIN.	TYP.	MAX.	UNIT
		OTHER	V _{CC} (V)				
T _{amb} = -40 to +125 °C							
V _{IH}	HIGH-level input voltage		2.0	1.5	-	-	V
			4.5	3.15	-	-	V
			6.0	4.2	-	-	V
V _{IL}	LOW-level input voltage		2.0	-	-	0.5	V
			4.5	-	-	1.35	V
			6.0	-	-	1.8	V
V _{OH}	HIGH-level output voltage	V _I = V _{IH} or V _{IL}	2.0	1.9	-	-	V
		I _O = -20 μA	4.5	4.4	-	-	V
		I _O = -20 μA	6.0	5.9	-	-	V
		I _O = -4.0 mA	4.5	3.7	-	-	V
		I _O = -5.2 mA	6.0	5.2	-	-	V
V _{OL}	LOW-level output voltage	V _I = V _{IH} or V _{IL}	2.0	-	-	0.1	V
		I _O = 20 μA	4.5	-	-	0.1	V
		I _O = 20 μA	6.0	-	-	0.1	V
		I _O = 4.0 mA	4.5	-	-	0.4	V
		I _O = 5.2 mA	6.0	-	-	0.4	V
I _{LI}	input leakage current	V _I = V _{CC} or GND	6.0	-	-	±1.0	μA
I _{OZ}	3-state output OFF current	V _I = V _{IH} or V _{IL} ; V _O = V _{CC} or GND	6.0	-	-	±10.0	μA
I _{CC}	quiescent supply current	V _I = V _{CC} or GND; I _O = 0	6.0	-	-	40	μA

Note

1. All typical values are measured at T_{amb} = 25 °C.

- These tell you:
 - Voltage ranges for valid 1 and 0 on input
 - Guaranteed output voltages as a function of load
 - How much load the gate input puts on the output of anything it is connected to

Key AC Characteristics



Philips Semiconductors

Product specification

Quad 2-input NAND gate

74HC00; 74HCT00

AC CHARACTERISTICS

Type 74HC00

GND = 0 V; $t_r = t_f = 6$ ns; $C_L = 50$ pF.

SYMBOL	PARAMETER	TEST CONDITIONS		MIN.	TYP.	MAX.	UNIT
		WAVEFORMS	V_{CC} (V)				
$T_{amb} = -40$ to $+85$ °C; note 1							
t_{PHL}/t_{PLH}	propagation delay nA, nB to nY	see Fig.6	2.0	–	25	115	ns
		see Fig.6	4.5	–	9	23	ns
		see Fig.6	6.0	–	7	20	ns
t_{THL}/t_{TLH}	output transition time		2.0	–	19	95	ns
			4.5	–	7	19	ns
			6.0	–	6	16	ns

 


Fig.6 Waveforms showing the input (nA, nB) to output (nY) propagation delays.

- Since this is ultimately an analog device it is essential to consider propagation delays in any array of gates
- The delays are compounded
- Parallel tracks in the logic equation give rise to races and glitches if you are not careful
- Often a clock function is used to allow a “settling time” and then to record (or “register” the output before proceeding to the next step in the device operation


Digital Signal Requirements



- Signals must never remain in “never-never land”. At a minimum this increases power draw and may damage the chip
- Transitions must be monotonic and “fast”
- Slow or sloppy transitions must be conditioned by triggers or discriminators
- If the signals are only slow, most logic families include devices with Schmidt trigger inputs
- Mechanical contacts must be de-bounced




Simple Memory – Set/Reset Flip-Flop

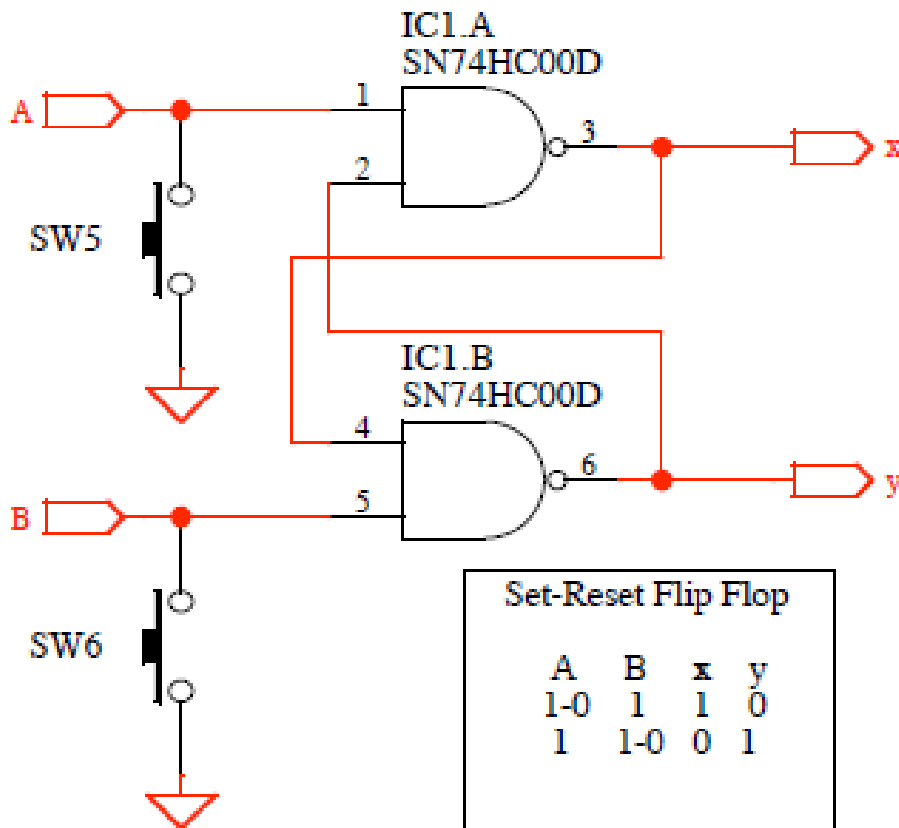


- Pushing a button sets (A) or resets (B) the device
- This state remains until the other button is pushed
- “Set” and “Reset” describe the device state – one output is always the complement of each other

The Clocked "D" Flip-Flop

 

Functional Diagram

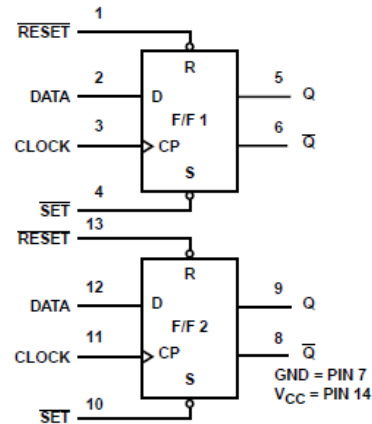

TRUTH TABLE


- On the leading edge of the clock, the state of D is remembered in the outputs
 - The state is remembered before the outputs change
- Therefore the outputs may be fed back into the logic that determines the input without ambiguity

INPUTS				OUTPUTS	
SET	RESET	CP	D	Q	Q̄
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H (Note 1)	H (Note 1)
H	H	↑	H	H	L
H	H	↑	L	L	H
H	H	L	X	Q0	Q̄0

H= High Level (Steady State) ↑= Low-to-High Transition
 L= Low Level (Steady State) Q0 = the level of Q before the indicated input conditions were established.
 X= Don't Care NOTE:


1. This configuration is nonstable, that is, it will not persist when set and reset inputs return to their inactive (high) level.

One-Shots

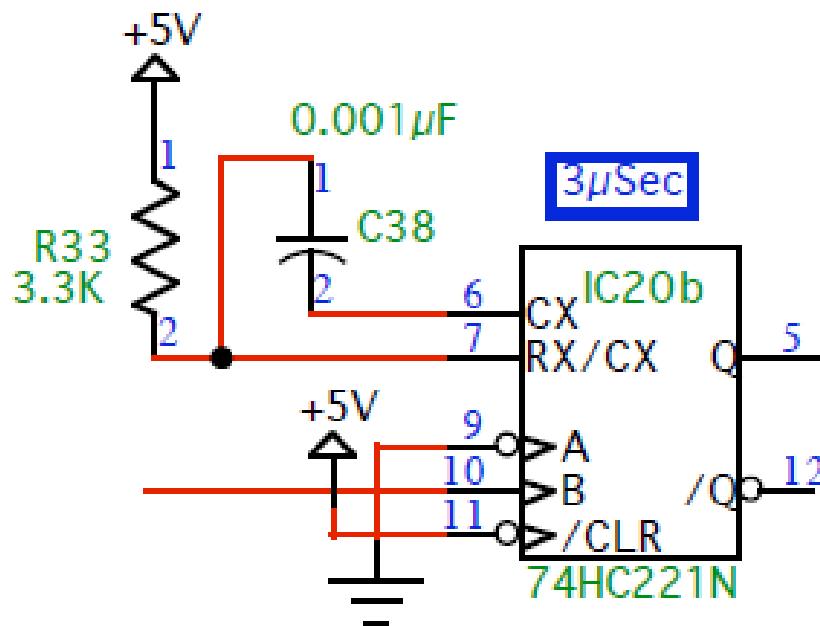

- A “one-shot” produces a pulse in response to a “leading edge” on the input
- The opposite transition produces no response
- If a precise (or very long) pulse duration is needed, use a device where this is controlled by analog components


Simple One-Shot for Edge Triggering

 

Add buffers or inverters (in pairs) here to lengthen the pulse


- Produces a short pulse on positive edge
- No reaction to the following negative edge
- Duration is a function of temperature, supply voltage, and device variation
- If implemented with devices in the same logic family the pulse is usually long enough with one inverter
- More buffers or inverters will lengthen it (to a point)

Ripple Counter from D Flip-Flops

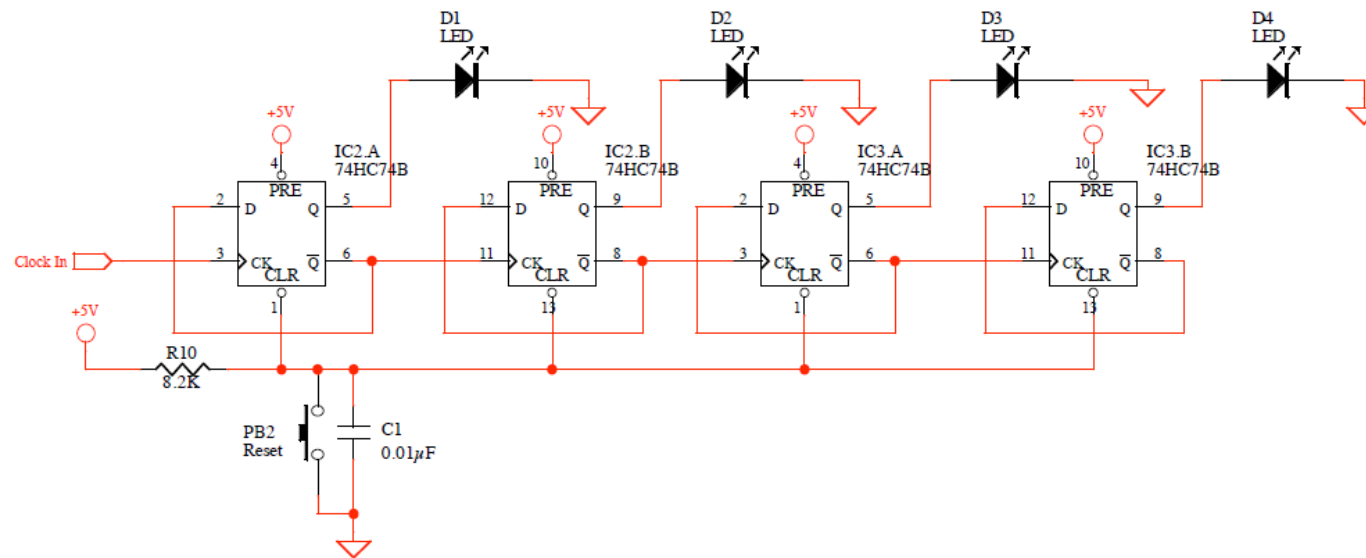

- When clocked, each D changes state because Qbar is fed back into D
- When and only when Qbar rises the next flipflop is clocked
- Each thus operates at half the rate of the previous stage forming a counter
- Because of the ripple, not all stages change state at the same time so the count is actually only well defined after a settling time
- Synchronous counters also exist, where all outputs change simultaneously
- Even there, the finite time of the transition can cause glitches


Shift Registers

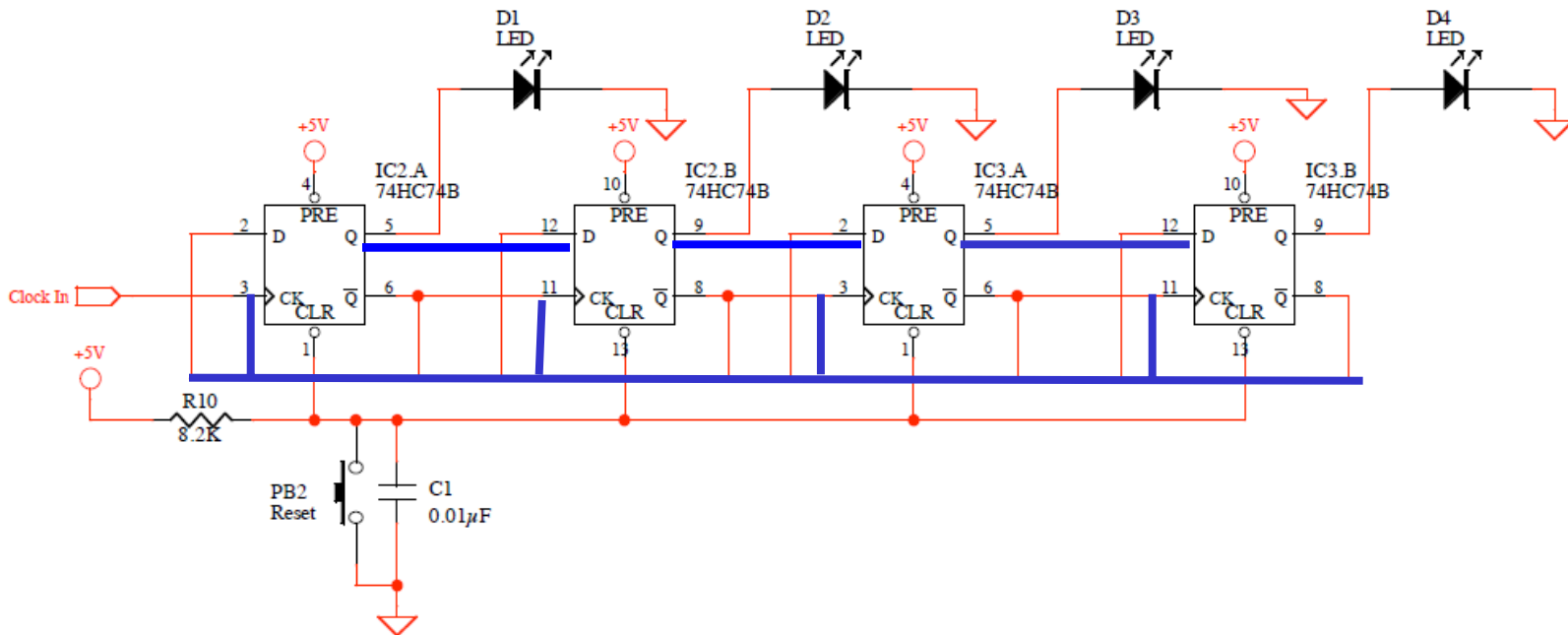

- The ripple counter becomes a “shift register” if Q of one stage is connected to D of the following, and all the clocks are connected together



Johnson Counter – Multiphase Clock

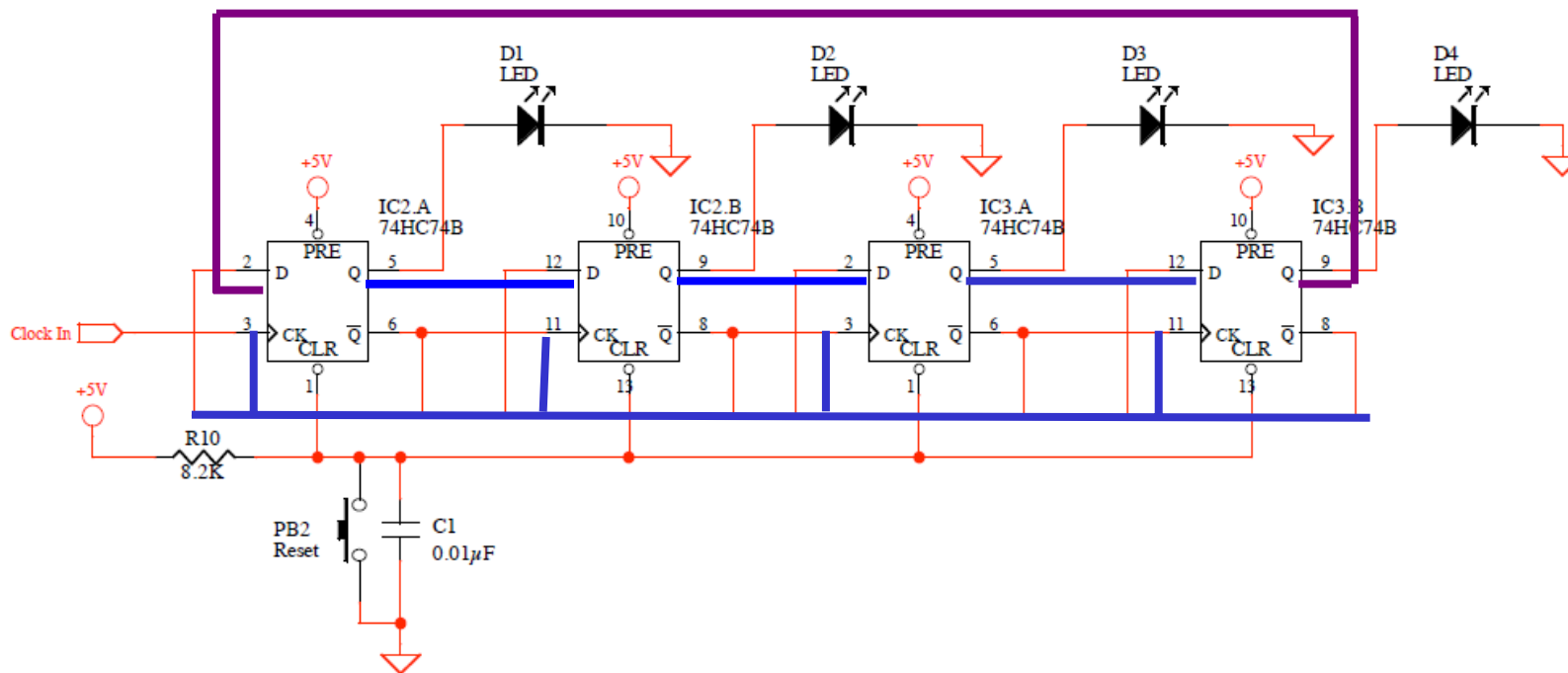


- A shift register loaded with a single “1” becomes what is known as a Johnson Counter
- The “1” moves from stage to stage, and is often the simplest way to sequence logic and allow for setup time
- Fed back on itself this becomes a “multiphase clock”
- Typically only the “even” phases are used to sequence logic, ensuring that there is no overlap and good settling time

Problem 1: Implement the following using only NAND gates




- Buffer
- Inverter
- AND
- OR
- XOR (Exclusive Or)

Problem 2: Explain How This Circuit “Debounces” the Contacts

 



Problem 3: How a D Flipflop Works

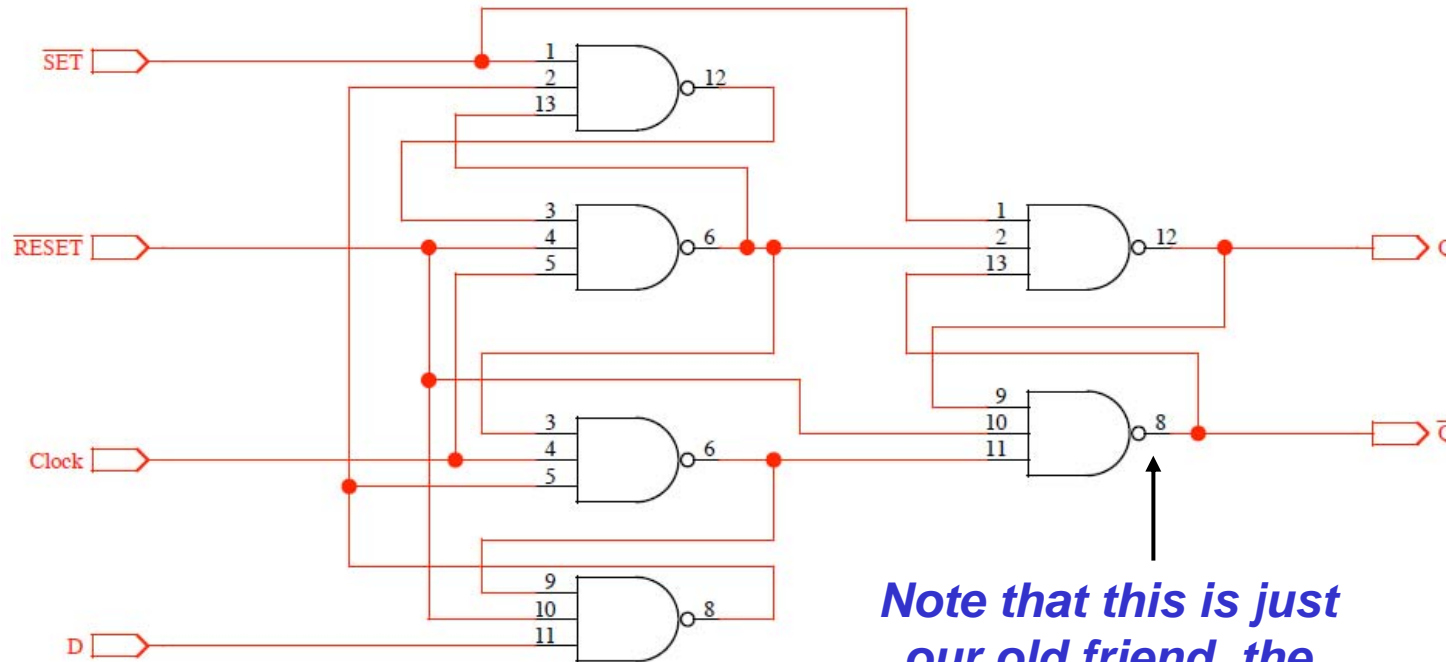


Note that this is just our old friend, the set-reset flipflop

- Figure out how gate delays implement the edge triggered feature of the D flipflop
- Using the chips on the prototype board build this circuit and use it to add one more stage to the counter



Problem 4: Design a Full Adder

 

Input			Output	
A	B	C _i	C _o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = (A \oplus B) \oplus C_{in}$$

$$C_{out} = (A \cdot B) + (C_{in} \cdot (A \oplus B)) = (A \cdot B) + (C_{in} \cdot B) + (C_{in} \cdot A)$$

Problem 5: Design an 8 Bit “Accumulator” to Add 4 Bit Numbers



- An accumulator is an array of memory cells to which successive numbers can be added
- Use four of the switches for input
- Use one of the push buttons as a clock
- Display the results in the lights


Problem 6: Design a Circuit to Multiply Two 4 Bit Numbers



- Multiplying two, four bit numbers yields an eight bit product
- This actually could be implemented with a lot of gates, since there is an 8 bit \rightarrow 8 bit truth table that uniquely specifies the answer, but here you should do it with clocked logic
- Use two groups of four switches for the inputs
- Display the product in the lights
- Use a push button to initiate the clock sequence




Problem 4: Answer

 

Full adder circuit diagram
Inputs: {A, B, CarryIn} → Outputs: {Sum, CarryOut}

Input			Output	
A	B	C_i	C_o	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 

$$S = (A \oplus B) \oplus C_{in}$$

$$C_{out} = (A \cdot B) + (C_{in} \cdot (A \oplus B)) = (A \cdot B) + (C_{in} \cdot B) + (C_{in} \cdot A)$$